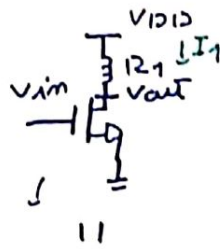




complete analysis

1st stage resistive common source stage

DC




In small signals

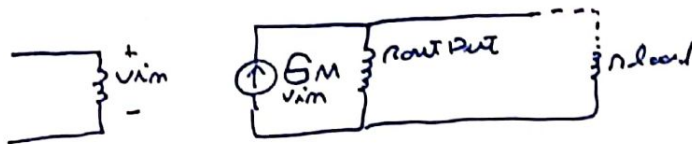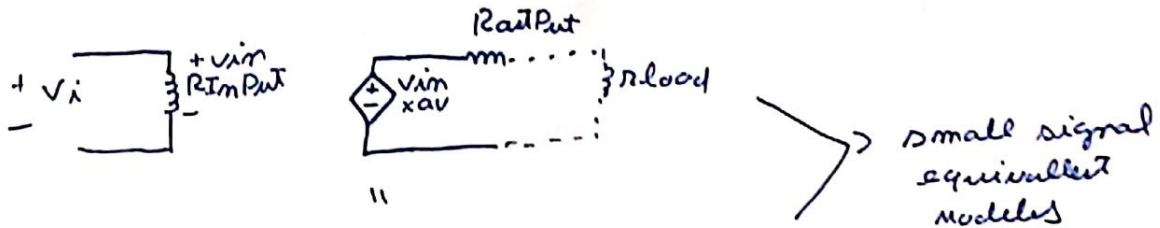

R_{inPut}


In MOS $R_{in} \approx 10^{15} \Omega$ and a capacitance generally since this is DC, the DC is Ignored
 $R_{inPut} \text{ (In DC and low frequencies)} = \infty$

R_{outPut}

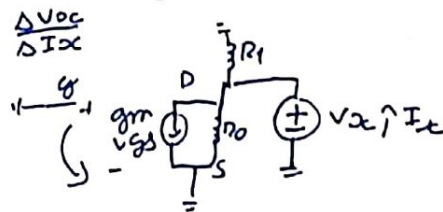

$$\frac{V_{oc}}{I_x} = R_1 || R_o = R_o$$

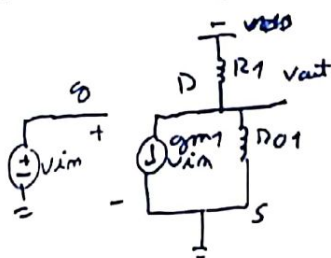AV Voltage gain $\frac{\Delta V_{out}}{\Delta V_{in}}$



$$\frac{V_{out}}{V_{in}} = \frac{-g_m R_1 R_o}{R_1 || R_o}$$


equivalent current gain

$$\frac{\Delta I_D}{\Delta v_{in}} = g_m$$

The Parameters for

The equivalent small frequency circuit

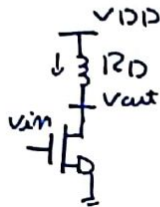In large signal assuming level 1 equations analysis, DC simulation



$$V_{GS} = v_{in}$$

$$V_{DS} = v_{out}$$

$$v_{out} = V_{DD} - I_D R_D$$

$$v_{out} = V_{DD} - I_D R_D$$
$$\frac{V_{DD} - v_{out}}{R_D} = I_D \text{ saturated}$$

} starting
In saturation

The Transistor enters in the Triode

when $V_{GS} - V_{th} > v_{out}$

↓

To make sure the Transistor stays the longest in saturation, we have to make sure the gain is the highest.

↓
As the result the gain becomes not linear, creates a lot of distortion


"longest" with v_{out} as reference

In the ~~new~~ Modern Process



I_D varies not in a quadratic way with changes in v_{in} , and its dependencies in Process Parameters are not as linear as they are in level 1 model

System analysis over frequency

resistive common source stage

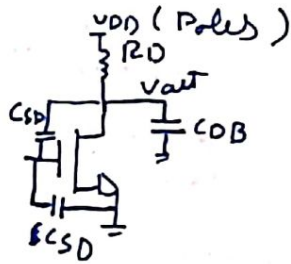

"
equivalent circuit

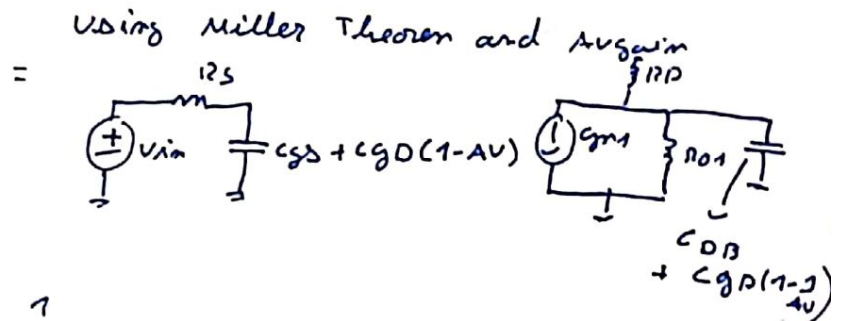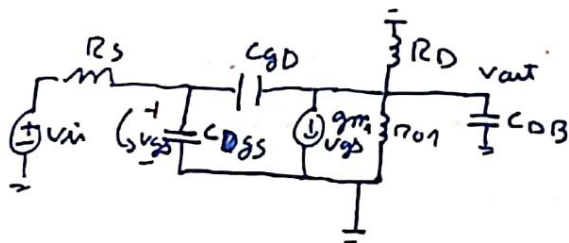


$$\omega_{in} = \frac{1}{R_S \times C_{eq}} = \frac{1}{R_S (C_{GS} + C_{GD}(1 + g_{m1} || r_{o1} || R_D))}$$

$$\omega_{out} = \frac{1}{\frac{R_D || r_{o1}}{R_{eq}} \times (C_{DB} + C_{GS}(1 - \frac{1}{A_V}))}$$

$$A_V(s) = A_V(\text{low frequency}) \times \frac{1}{(1 + \frac{s}{\omega_{in}})(1 + \frac{s}{\omega_{out}})}$$

The "easy way" to calculate

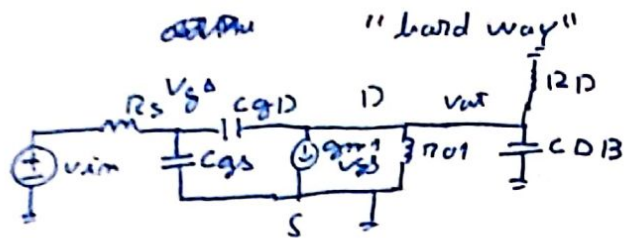

$$Z_{eq1} = R_D \parallel r_{o1} \parallel \frac{1}{C_{DB} s}$$

$$Z_{eq1} = \frac{R_D r_{o1}}{R_D + r_{o1}} \parallel \frac{1}{C_{DB} s}$$

$$Z_{eq1} = \frac{\frac{R_D r_{o1}}{R_D + r_{o1}}}{\frac{R_D r_{o1}}{R_D + r_{o1}} + \frac{1}{C_{DB} s}}$$

$$Z_{eq1} = \frac{R_D r_{o1}}{(R_D + r_{o1}) C_{DB} s}$$

$$Z_{eq1} = \frac{R_D r_{o1}}{(R_D + r_{o1}) C_{DB} s + (r_{o1} + r_{o1})}$$

$$V_{GS} (C_{GS} s) + \frac{V_{GS} - v_{in}}{R_S} + (V_{GS} - v_{out}) C_{GD} = 0$$

$$\frac{v_{out}}{Z_{eq1}} + g_m V_{GS} + (v_{out} - V_{GS}) C_{GD} s = 0$$

$$-v_{out} \left(\frac{1}{Z_{eq1}} + C_{GD} s \right) = V_{GS} (g_m - C_{GD} s)$$

$$-v_{out} \left(C_{GD} s + \left(\frac{1}{Z_{eq1}} + C_{GD} s \right) \right) \left(C_{GD} s + \frac{1}{R_S} + C_{GD} s \right) = \frac{v_{in}}{R_S}$$


$$A_V(s) = \frac{+ \left(\frac{1}{R_S} \right) (-g_m + C_{GD} s)}{(C_{GD} s)(g_m - C_{GD} s) + \frac{1}{Z_{eq1}} + (C_{GD} s) (\dots)}$$

$$A_V(s) = \frac{R_S Z_{eq1} (-g_m + C_{GD} s)}{R_S Z_{eq1} (C_{GD} s)(g_m - C_{GD} s) + (1 + C_{GD} s)(1 + R_S (C_{GD} s + C_{GD} s))}$$

↓ continue this will result

In a second order equation with two poles
→ Its hard to solve

output Impedance

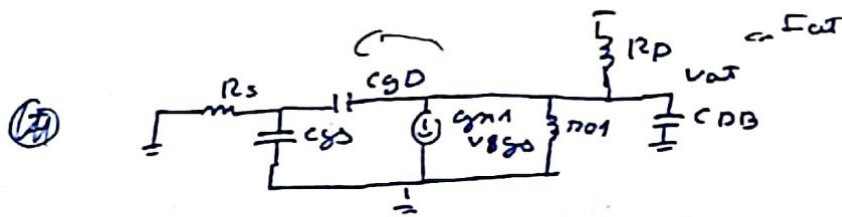

$$Z_{eq1} = R_D \parallel R_{o1} \parallel \frac{1}{C_{DBD}} = \frac{R_D R_{o1}}{(R_D R_{o1}) C_{DBD} + (R_D + R_{o1})}$$

$$V_{gs} = \frac{R_S \parallel \frac{1}{C_{gD0}}}{R_S \parallel \frac{1}{C_{gD0}} + \frac{1}{C_{gD0}}} \times V_{out}$$

$$R_S \parallel \frac{1}{C_{gD0}} = \frac{R_S}{R_S C_{gD0} + 1}$$

$$\frac{R_S C_{gD0} (R_D R_{o1} + 1)}{(R_S C_{gD0} + 1) C_{gD0}}$$


$$V_{gs} = \frac{R_D C_{gD0}}{R_D C_{gD0} + (R_D C_{gD0} + 1)} \times V_{out}$$

$$Z_{eq2}$$

$$\frac{V_{out}}{Z_{eq1}} + g_{m1} V_{gs} + (V_{out} - V_{gs}) C_{gD0} = I_{out}$$

$$V_{out} \left(\frac{1}{Z_{eq1}} + g_{m1} Z_{eq2} + C_{gD0} - Z_{eq2} C_{gD0} \right) = I_{out}$$
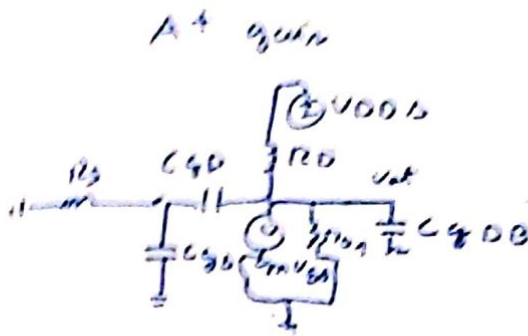
$$\frac{I_{out}}{V_{out}} = \frac{1}{Z_{eq1}} \frac{1}{(1 + Z_{eq1} Z_{eq2} g_{m1} + C_{gD0} Z_{eq1} - Z_{eq2} Z_{eq1} C_{gD0})}$$



$$A_1 = \frac{V_{out}}{V_{in}}$$

$$V_{gs} = V_{in} Z_{in2}$$

$$Z_{in1} = \frac{1}{C_{GD}} \parallel R_{o1} = \frac{R_{o1}}{R_{o1}C_{GD}s + 1}$$

$$\frac{R_{o1}}{C_{GD}s + 1} \parallel \frac{R_{o1}C_{GD}s + 1}{C_{GD}s + 1} = \frac{R_{o1}}{R_{o1}C_{GD}s + 1}$$

$$\frac{V_{out} - V_{DD}}{R_{DD}} + \frac{V_{out}}{Z_{in1}} + g_m V_{gs} V_{DD} + (V_{out} - V_{gs}) C_{GD} s = 0$$

$$V_{out} \left(\frac{1}{R_D} + \frac{1}{Z_{in1}} + C_{GD} s + Z_{in1} (g_m - C_{GD} s) \right) = \frac{V_{DD}}{R_D}$$

$$\frac{V_{out}}{V_{DD}} = A_1 = \frac{1}{R_D}$$

$$\frac{\frac{1}{R_D}}{\frac{1}{R_D} + \frac{1}{R_{o1}}} = \frac{1}{1 + \frac{R_D}{R_{o1}}} = \frac{R_{o1}}{R_{o1} + R_D} \rightarrow \text{At low frequencies}$$

con. line
obtained
By $A_1(s)$


Low frequency gain

$$\frac{V_{out} - V_{DD}}{R_D} + \frac{V_{out}}{R_{o1}} = 0$$

$$-\frac{V_{DD}}{R_D} = -V_{out} \left(\frac{1}{R_D} + \frac{1}{R_{o1}} \right)$$

$$\frac{V_{out}}{V_{DD}} = \frac{1}{R_D} \div \left(\frac{1}{R_{o1}} + \frac{1}{R_D} \right) = \frac{R_{o1}}{R_{o1} + R_D}$$

A - gain

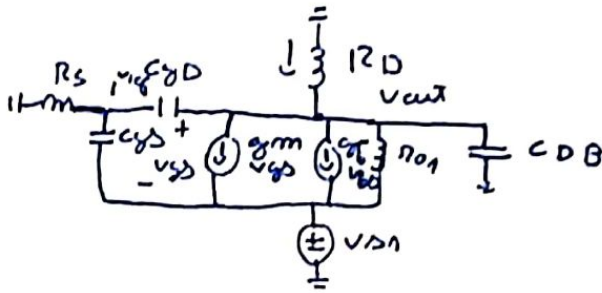

$$Z_{eq1} = R_D \parallel \frac{1}{C_{DBs}}$$

$$= \frac{R_D}{R_D C_{DBs} + 1}$$

$$-\frac{V_{out}}{Z_{eq1}} = \frac{V_{out} - V_{DS}}{r_{o1}} + g_m V_{gs} + (V_{out} - V_g) C_{DBs} + g_m V_{DS} - V_{DS}$$

$$V_{gs} = V_g - V_{DS}$$

$$\frac{V_g}{R_D} + (V_g - V_{out}) C_{DBs} + (V_g - V_{DS}) C_{DBs} = 0$$

$$V_g \left(\frac{1}{R_D} + C_{DBs} + C_{DBs} \right) = V_{out} C_{DBs} + V_{DS} C_{DBs}$$

$$V_g = \frac{V_{out} C_{DBs} + V_{DS} C_{DBs}}{\left(\frac{1}{R_D} + C_{DBs} + C_{DBs} \right)}$$

$$-\frac{V_{out}}{Z_{eq1}} = \frac{V_{out} - V_{DS}}{r_{o1}} + g_m (V_g - V_{DS}) + (V_{out} - V_g) C_{DBs} + g_m (-V_{DS})$$

$$+ V_{out} \left(\frac{1}{Z_{eq1}} + C_{DBs} + \frac{C_{DBs}}{\left(\frac{1}{R_D} + C_{DBs} + C_{DBs} \right)} (g_m - C_{DBs}) + \frac{1}{r_{o1}} \right)$$

$$= + V_{DS} \left(\frac{1}{r_{o1}} + g_m + \frac{C_{DBs}}{\left(\frac{1}{R_D} + C_{DBs} + C_{DBs} \right)} (C_{DBs} - g_m) \right)$$

$$\frac{V_{out}}{V_{DS}} = \frac{\left(\frac{1}{r_{o1}} + g_m + \frac{C_{DBs}}{\left(\frac{1}{R_D} + C_{DBs} + C_{DBs} \right)} (C_{DBs} - g_m) + g_m \right)}{\left(\frac{1}{Z_{eq1}} + C_{DBs} + \frac{1}{r_{o1}} + \frac{C_{DBs}}{\left(\frac{1}{R_D} + C_{DBs} + C_{DBs} \right)} (C_{DBs} - g_m) \right)}$$